

# Kirchoff's laws, Ohm's Law, and Circuit Analysis



# Kirchoff's voltage law

- Electric potential difference is also referred to as voltage
- Kirchoff's Voltage Law:
  - In any complete path in an electric circuit, the total electric potential increase at the source(s) is equal to the total electric potential decrease throughout the rest of the circuit
  - $V_{\text{series}} = V_1 + V_2 + V_3 + \dots$
  - $V_{\text{parallel}} = V_1 = V_2 = V_3 = \dots$




# Kirchoff's Current Law

- In electric circuits, junctions are points where the current can split to follow more than one path
- Kirchhoff's Current Law:
  - In a closed circuit, the amount of current entering a junction is equal to the amount of current exiting a junction.
  - $I_{\text{series}} = I_1 = I_2 = I_3 = \dots\dots\dots$
  - $I_{\text{parallel}} = I_1 + I_2 + I_3 + \dots\dots\dots$



# Practice questions Pg. 522

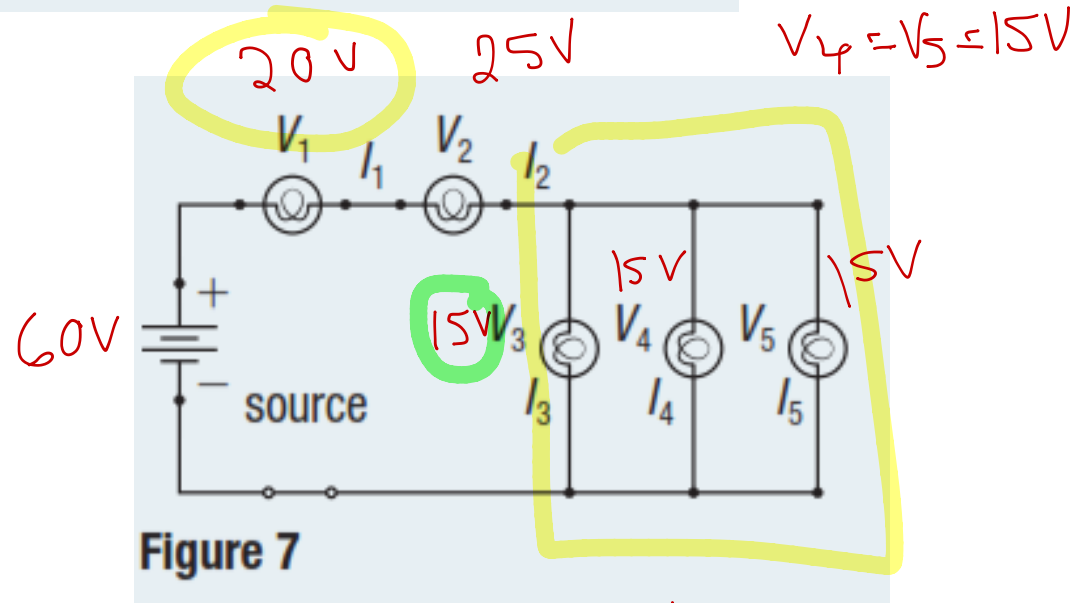1. For the circuit in **Figure 7**,  $V_{\text{source}} = 60.0 \text{ V}$ ,  $V_1 = 20.0 \text{ V}$ , and  $V_3 = 15 \text{ V}$ . Determine  $V_2$ ,  $V_4$ , and  $V_5$ . **T/A** [ans:  $V_2 = 25 \text{ V}$ ;  $V_4 = 15 \text{ V}$ ;  $V_5 = 15 \text{ V}$ ]




$$V_2 = 60 \text{ V} - 20 \text{ V} - 15 \text{ V}$$

$$V_2 = 25 \text{ V}$$



# More Practice Problems Pg. 522

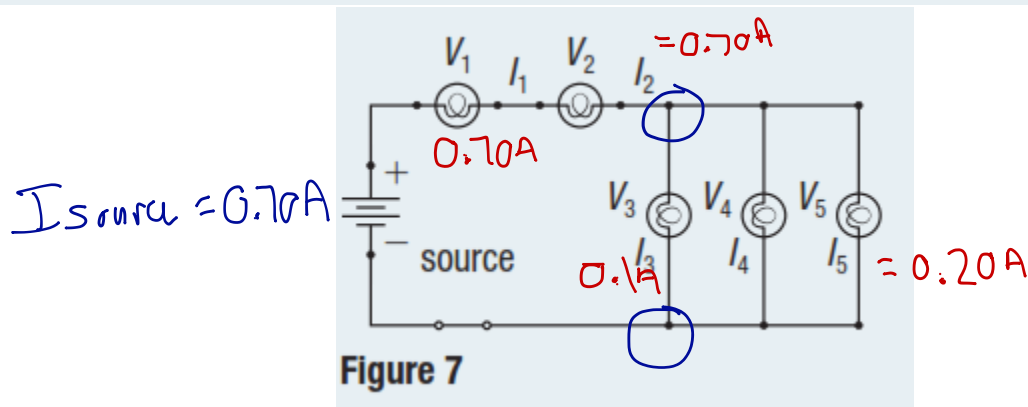2. For the circuit in Figure 7,  $I_1 = 0.70 \text{ A}$ ,  $I_3 = 0.10 \text{ A}$ , and  $I_5 = 0.20 \text{ A}$ . Determine  $I_{\text{source}}$ ,  $I_2$ , and  $I_4$ . [ans:  $I_{\text{source}} = 0.70 \text{ A}$ ;  $I_2 = 0.70 \text{ A}$ ;  $I_4 = 0.40 \text{ A}$ ]




$$I_4 = 0.7 - (0.1 + 0.2)$$

$$I_4 = 0.40 \text{ A}$$


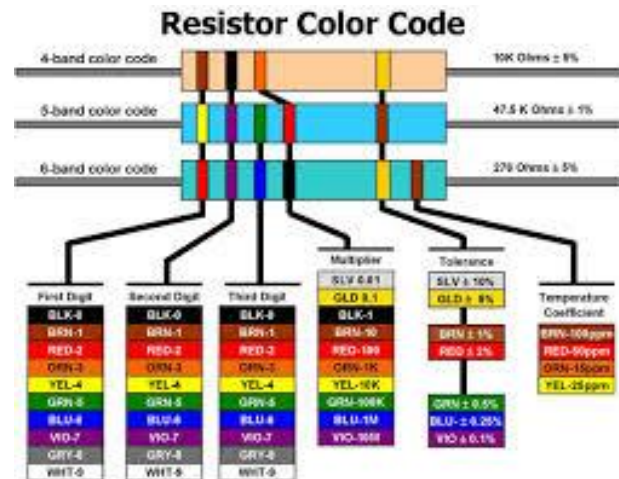
# Electrical resistance

- Electrical resistance (R):
  - a property of matter that describes how difficult it is for electric current to travel through a material
- Resistor
  - an electrical device that has a specific resistance value



# Ohm's law

- The voltage in a conductor is proportional to the current if the temperature remains constant.

$$R = \frac{V}{I}$$

$$V = IR$$



# Ohm's Law

- R
  - resistance measured in volts per ampere ( ohms)
- V
  - voltage measured in volts (V)
- I
  - electric current measured in amperes or amps (A)






# Measuring resistance

- Ohmmeter
  - a device that measures electrical resistance
  - connected in parallel and **must never** be used on a live circuit



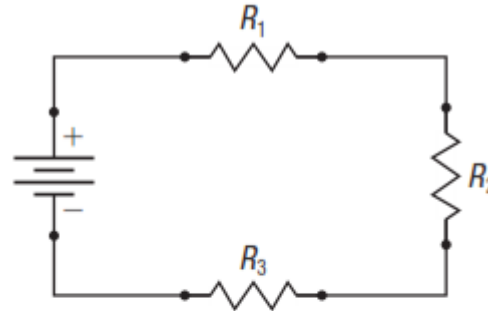
# Resistors in circuits

- Resistors in Series
  - substitute Ohm's Law into KVL
  - generates an equivalent resistance
  - $R_{\text{series}} = R_1 + R_2 + R_3 + \dots$




↓  
can be reduced to

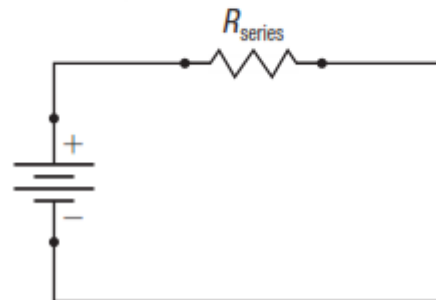

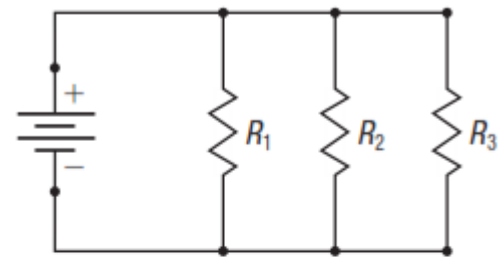
# Resistors in circuits

- Resistors in parallel
  - Substitute Ohm's Law (isolate I) into KCL
  - generate an equivalent resistance
  - Equation:  $\frac{1}{R_{parallel}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$



↓ can be reduced to

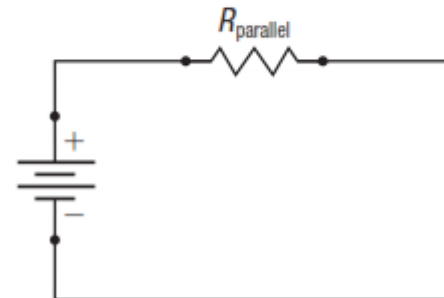

# Example #1

- Determine the equivalent resistance for a 25.2 ohm resistor connected in series with a 28.12 ohm resistor.

$$R_T = 25.2 \Omega + 28.12 \Omega$$

$$\begin{array}{r} 25.2 \\ 28.12 \\ \hline 53.32 \end{array}$$

$$R_T = 53.3 \Omega$$



## Example #2

- Determine the equivalent resistance of a 120 ohm resistor connected in parallel with a 60 ohm resistor.

$$\begin{aligned}\frac{1}{R_{eq}} &= \frac{1}{120\Omega} + \frac{1}{60\Omega} \\ &= \frac{1}{120\Omega} + \frac{2}{120\Omega} \\ \frac{1}{R_{eq}} &= \frac{3}{120\Omega} \\ R_{eq} &= 120\Omega / 3 = 40\Omega\end{aligned}$$



# Equivalent resistance in mixed circuits

## Practice

Pg 530

1. What is the total resistance of the mixed circuits shown in **Figure 6**? Note that each resistor has resistance  $5.0\ \Omega$ . T/N [ans: (a)  $17.5\ \Omega$ ; (b)  $6.3\ \Omega$ ]


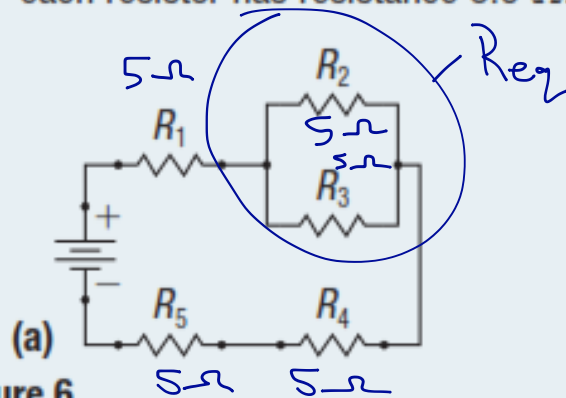


Figure 6

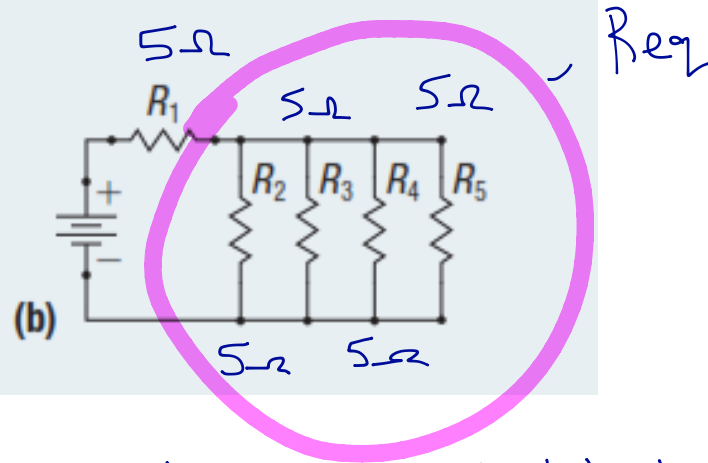

$$\frac{1}{R_{eq}} = \frac{1}{5\Omega} + \frac{1}{5\Omega}$$

$$\frac{1}{R_{eq}} = \frac{2}{5\Omega}$$

$$R_{eq} = \frac{5\Omega}{2} = 2.5\Omega$$

$$R_T = 5\Omega + 2.5\Omega + 5\Omega + 5\Omega$$

$$R_T = 17.5\Omega$$

$$\frac{1}{R_{eq}} = \frac{1}{5\Omega} + \frac{1}{5\Omega} + \frac{1}{5\Omega} + \frac{1}{5\Omega}$$

$$\frac{1}{R_{eq}} = \frac{4}{5\Omega}$$

$$R_{eq} = \frac{5\Omega}{4} = 1.25\Omega$$

$$R_T = 5\Omega + 1.25\Omega$$

$$R_T = 6.25\Omega$$

# Work

- Read 11.7, 11.8, and 11.9
- Pg. 527 #2
- Pg. 529 #2
- Pg. 530 #5
- ~~▪ Pg. 535 #1b~~

