

Kirchoff's laws, Ohm's Law, and Circuit Analysis



Circuit analysis


- To analyse a circuit means to find all the unknown values of voltage, current, and resistance.
- Use a combination of equivalent resistance, Kirchoff's laws, and Ohm's Law.



Circuit analysis Example

1. For each of the circuit diagrams below, the source has a voltage of 6.0 V. Each resistor has resistance 12.0 Ω . Find all the other values of current, voltage, and resistance.

(a)

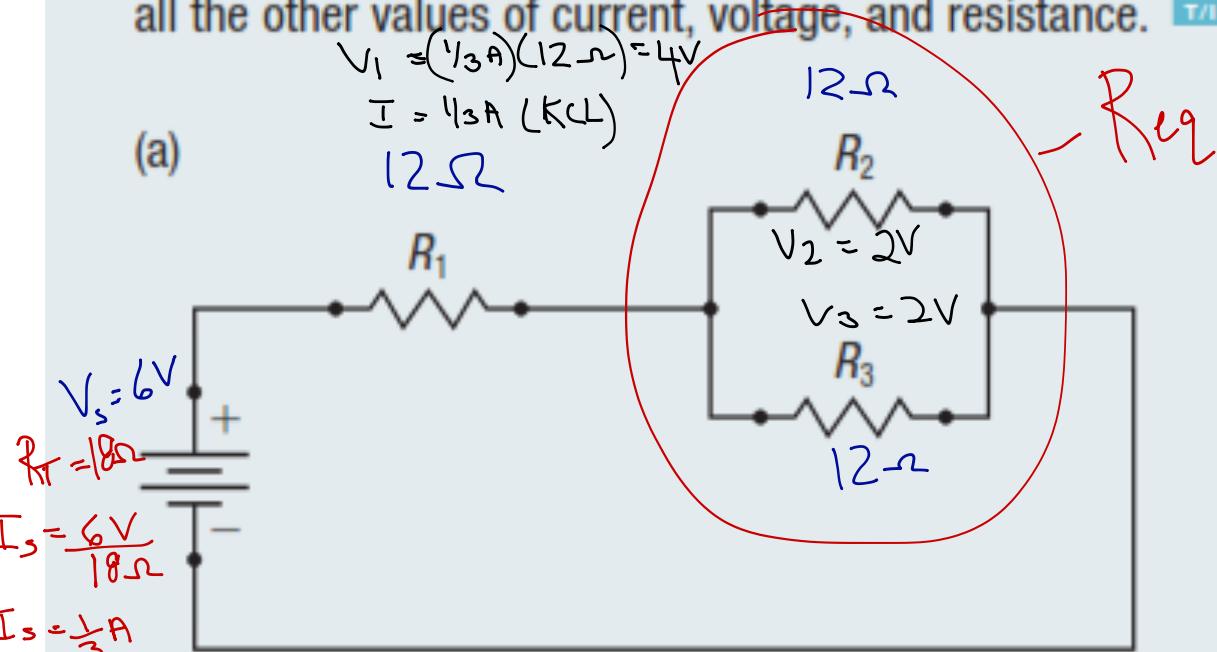

	V	I	R
Source	6V	$\frac{1}{3}A$	18Ω
1	4V	$\frac{1}{3}A$	12Ω
2	2V	$\frac{1}{6}A$	12Ω
3	2V	$\frac{1}{6}A$	12Ω

$$I_2 = I_3 = \frac{2V}{12\Omega} = \frac{1}{6}A$$

$$\begin{aligned} R_T &= 12\Omega + R_{eq} \\ R_T &= 12\Omega + 6\Omega \\ R_T &= 18\Omega \end{aligned}$$

$$\begin{aligned} \frac{1}{R_{eq}} &= \frac{1}{12\Omega} + \frac{1}{12\Omega} \\ \frac{1}{R_{eq}} &= \frac{2}{12} = \frac{1}{6\Omega} \\ R_{eq} &= 6\Omega \end{aligned}$$

$$R_1 = \frac{2.5V}{0.2A} = 12.5\Omega$$


$$R_3 = \frac{5V}{0.5A} = 10\Omega$$

$$I_3 = 0.5A$$

$$V_3 = 5V$$



Pg 535 #4

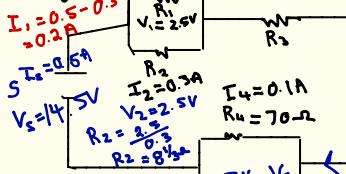

$$V_4 = (0.1A)(70\Omega) = 7V$$

$$V_4 = 7V$$

$$V_4 = V_S = 7V$$

Source	V	I	R
1	2.5V	0.2A	12.5Ω
2	2.5V	0.3A	8.33Ω
3	5V	0.5A	10Ω
4	7V	0.1A	70Ω
5	7V	0.4A	17.5Ω

$$V_S = 2.5V + 5V + 7V$$

$$V_S = 14.5V$$

$$R_S = \frac{V_S}{I_S}$$

$$= \frac{7V}{0.4A}$$

$$R_S = 17.5\Omega$$

$$R_T = \frac{14.5V}{0.5A}$$

$$R_T = 29\Omega$$

Work

- Read 11.7, 11.8, and 11.9
- Pg. ~~527~~ #2
- Pg. ~~529~~ #2
- Pg. ~~530~~ #5
- Pg. 535 #1b,_{c,d} #2, #3

Quiz Tomorrow

Circuits

V
H
R

