

RESISTANCE AND CIRCUIT ANALYSIS

KIRCHOFF'S VOLTAGE LAW

- Electric potential difference is also referred to as voltage
- Kirchoff's Voltage Law:
 - In any complete path in an electric circuit, the total electric potential increase at the source(s) is equal to the total electric potential decrease throughout the rest of the circuit
 - $V_{\text{series}} = V_1 + V_2 + V_3 + \dots$
 - $V_{\text{parallel}} = V_1 = V_2 = V_3 = \dots$




KIRCHOFF'S CURRENT LAW

- In electric circuits, junctions are points where the current can split to follow more than one path
- Kirchoff's Current Law:
 - In a closed circuit, the amount of current entering a junction is equal to the amount of current exiting a junction.
 - $I_{\text{series}} = I_1 = I_2 = I_3 = \dots$
 - $I_{\text{parallel}} = I_1 + I_2 + I_3 + \dots$



ELECTRICAL RESISTANCE

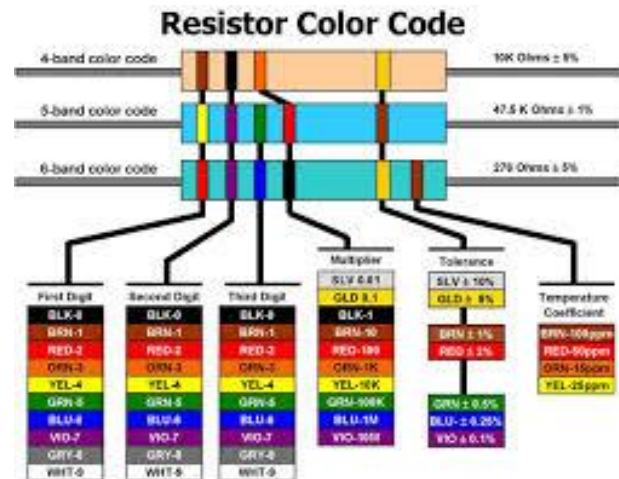- Electrical resistance (R):
 - a property of matter that describes how difficult it is for electric current to travel through a material
- Resistor
 - an electrical device that has a specific resistance value




OHM'S LAW

- The voltage in a conductor is proportional to the current if the temperature remains constant.

$$R = \frac{V}{I}$$

$$R = \frac{\Delta V}{I}$$

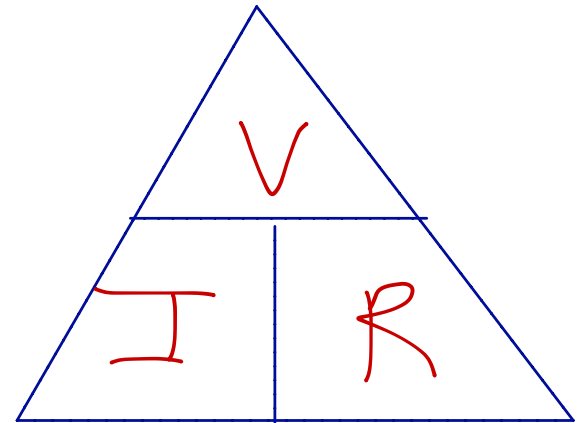

OHM'S LAW

- R
 - resistance measured in volts per ampere (ohms)
- V
 - voltage measured in volts (V)
- I
 - electric current measured in amperes or amps (A)



MEASURING RESISTANCE

○ Ohmmeter

- a device that measures electrical resistance
- connected in parallel and **must never** be used on a live circuit



EXAMPLE # 1 – CALCULATING RESISTANCE

- Calculate the resistance if the voltage drop is 12.0 V and the current is 8.0 mA.

Given: $V = 12.0 \text{ V}$


$$I = 8.0 \text{ mA} \\ = 0.008 \text{ A}$$

Unknown: $R = \text{resistance}$

Step:

$$R = \frac{V}{I} \\ = \frac{12 \text{ V}}{0.008 \text{ A}}$$

↑
must be in amps

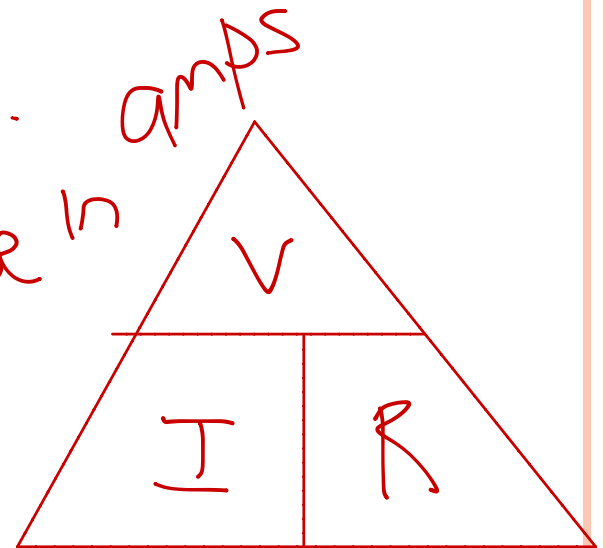

$$\therefore R = 1500 \Omega$$

↑
Symbol for
ohms

EQUIVALENT RESISTANCE


- A single resistance that can replace all the resistances in an electrical circuit while maintaining the same current when connected to the same source
- Symbol is R_{total} or R_t




RESISTORS IN CIRCUITS

○ Resistors in Series

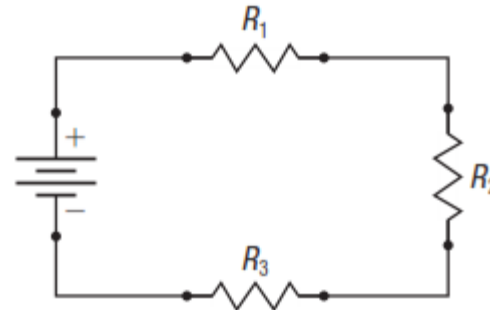- substitute Ohm's Law into KVL
- generates an equivalent resistance
- $R_t = R_{\text{series}} = R_1 + R_2 + R_3 + \dots$



↓ can be reduced to

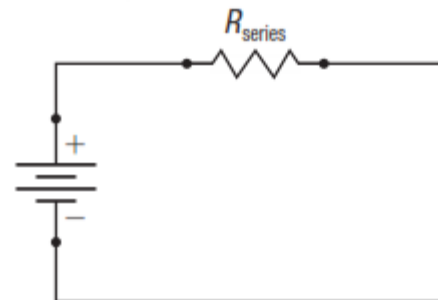


RESISTORS IN CIRCUITS


○ Resistors in parallel

- Substitute Ohm's Law (isolate I) into KCL
- generate an equivalent resistance

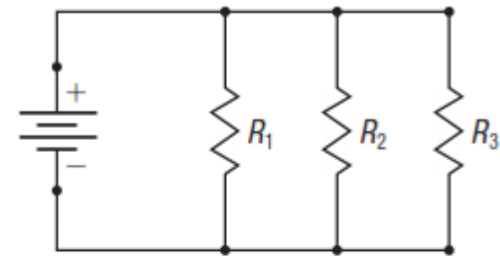• Equation:
$$\frac{1}{R_t} = \frac{1}{R_{parallel}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$




↓ can be reduced to

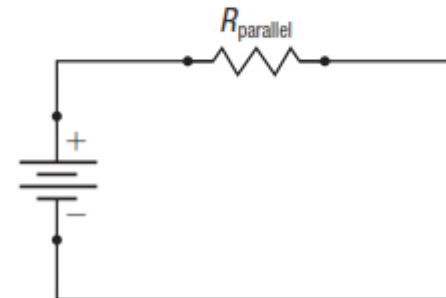

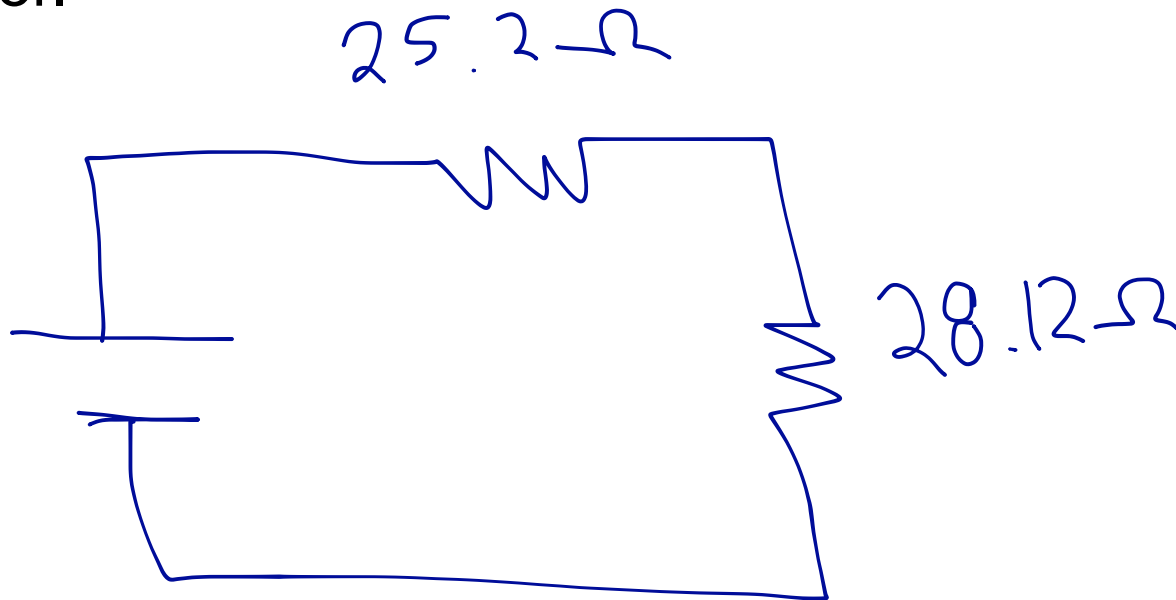EXAMPLE #2

- Determine the equivalent resistance for a 25.2 ohm resistor connected in series with a 28.12 ohm resistor.



$$R_T = 25.2 \Omega + 28.12 \Omega$$
$$R_T = 53.3 \Omega$$



EXAMPLE #3

- Determine the equivalent resistance of a 120 ohm resistor connected in parallel with a 60 ohm resistor.



$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{1}{120} + \frac{1}{60}$$

$$\frac{1}{R_T} = \frac{1}{120} + \frac{2}{120}$$

$$\frac{1}{R_T} = \frac{3}{120}$$

$$R_T = \frac{120}{3}$$

$$R_T = 40\Omega$$

