

RESISTANCE AND CIRCUIT ANALYSIS

EQUIVALENT RESISTANCE IN MIXED CIRCUITS

Practice

1. What is the total resistance of the mixed circuits shown in **Figure 6**? Note that each resistor has resistance 5.0Ω . T71 [ans: (a) 17.5Ω ; (b) 6.3Ω]


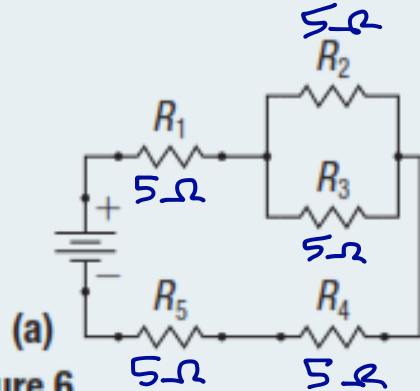


Figure 6

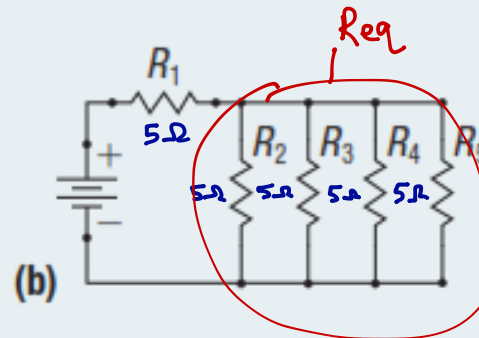

$$R_T = R_1 + R_{eq}$$

$$= 5\Omega + \frac{5\Omega}{4}$$

$$= 5\Omega + 1.25\Omega$$

$$R_T = 6.25\Omega$$

$$\begin{aligned} R_T &= R_1 + R_{eq} + R_4 + R_5 \\ &= 5\Omega + \frac{5\Omega}{2} + 5\Omega + 5\Omega \\ R_T &= 17.5\Omega \end{aligned}$$





CIRCUIT ANALYSIS

- To analyse a circuit means to find all the unknown values of voltage, current, and resistance.
- Use a combination of equivalent resistance, Kirchoff's laws, and Ohm's Law.



CIRCUIT ANALYSIS EXAMPLE

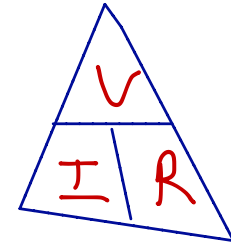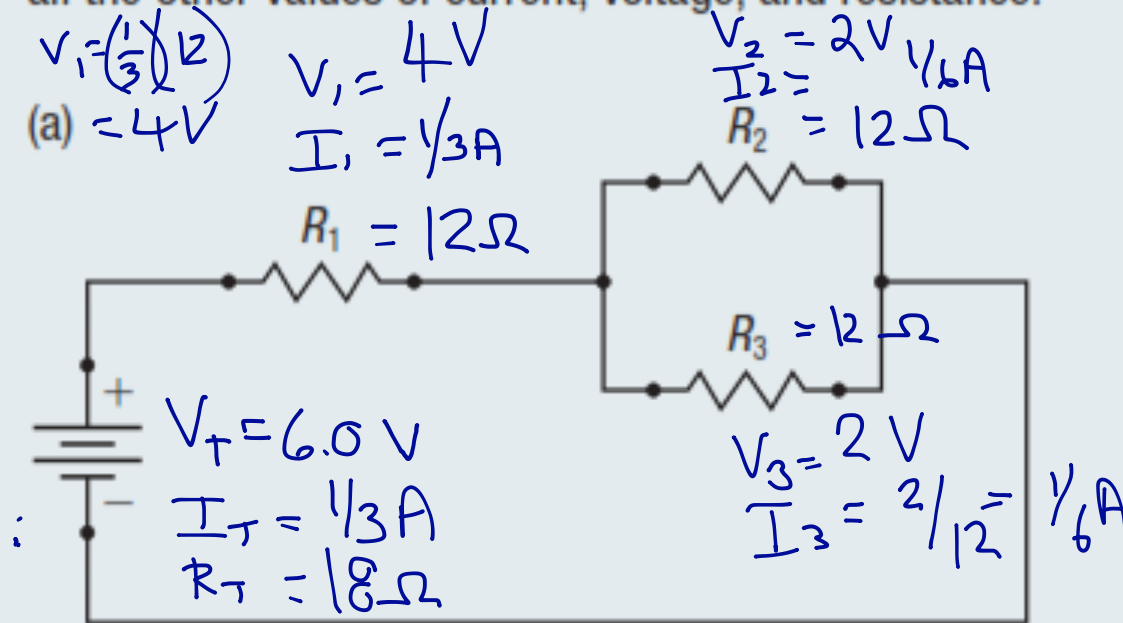1. For each of the circuit diagrams below, the source has a voltage of 6.0 V. Each resistor has resistance 12.0 Ω . Find all the other values of current, voltage, and resistance. T/1




	V	I	R
1	4V	$\frac{1}{3}A$	12 Ω
2	2V	$\frac{1}{6}A$	12 Ω
3	2V	$\frac{1}{6}A$	12 Ω
T	6.0V	$\frac{1}{3}A = 0.33A$	18 Ω

$$\begin{aligned}
 R_T &= R_1 + R_{eq} \\
 &= 12\Omega + 12/2 \\
 &= 18\Omega
 \end{aligned}$$
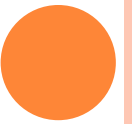
$$\begin{aligned}
 I_T &= \frac{V_T}{R_T} \\
 &= \frac{6}{18} = 0.33A
 \end{aligned}$$





WORK

- Read 7.4 and 7.6

- Pg. 337 # 1,2

- Pg. 339 # 4,6 — Yesterday

- Pg. 340 #7 → Yesterday

- Pg. 342 #9 → $\frac{1}{R_{eq}} = \frac{1}{R_2} + \frac{1}{R_3}$

