

Unit Test #1 - Electricity and Magnetism

C1.4	/13
C2.2	/10
C1.1	/13
C2.3	/13

Name: \_\_\_\_\_



**Instructions:**

1. Read each question carefully before answering.
2. Express all final answers with the correct number of significant digits.
3. Calculators may not be shared. No iPod or Smartphone calculators.
4. Good Luck !!

/13	C1.4	I can construct, or deconstruct, and explain the components of a basic electric device.
-----	------	---

1. What 3 basic parts are required in any electric circuit? Use correct terminology. Not examples. (3 marks)

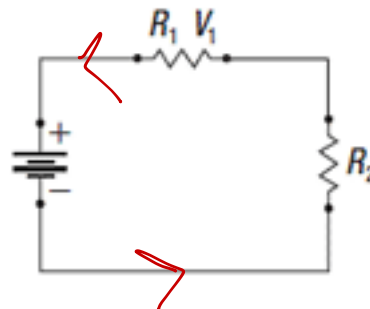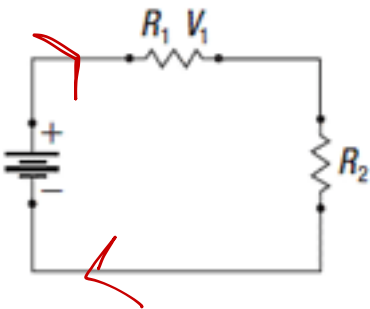2. In the circuit below left show the direction of conventional current flow, and on the circuit below right show the direction of electron flow. (2 marks)



3. Draw a circuit including a power source with 3 light bulbs connected in series. (4 marks)

4. Draw a circuit including a power source with 3 light bulbs connected in parallel. (4 marks)

/ 10	C2.2	I can compare and contrast the behaviour and functions of series, parallel, and mixed DC circuits.
------	------	--

5. Calculate the total electric potential difference across three 6.0 V batteries:

a) connected in series (2 marks)

b) connected in parallel (2 marks)


6. Determine the equivalent resistance when a 4.0Ω light bulb and a 8.0 Ω are:

a) connected in series (3 marks)


b) connected in parallel (3 marks)

/ 13	C1.1	I can construct DC circuits and analyse them using Ohm's law and Kirchoff's laws.
------	------	---

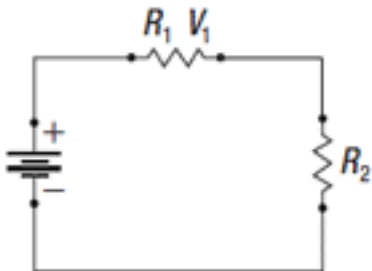7. The circuit below carries a current of 0.2A.  $V_1 = 6.2V$  and  $V_{source} = 15V$ . Determine the resistance of  $R_2$ . (3 marks)



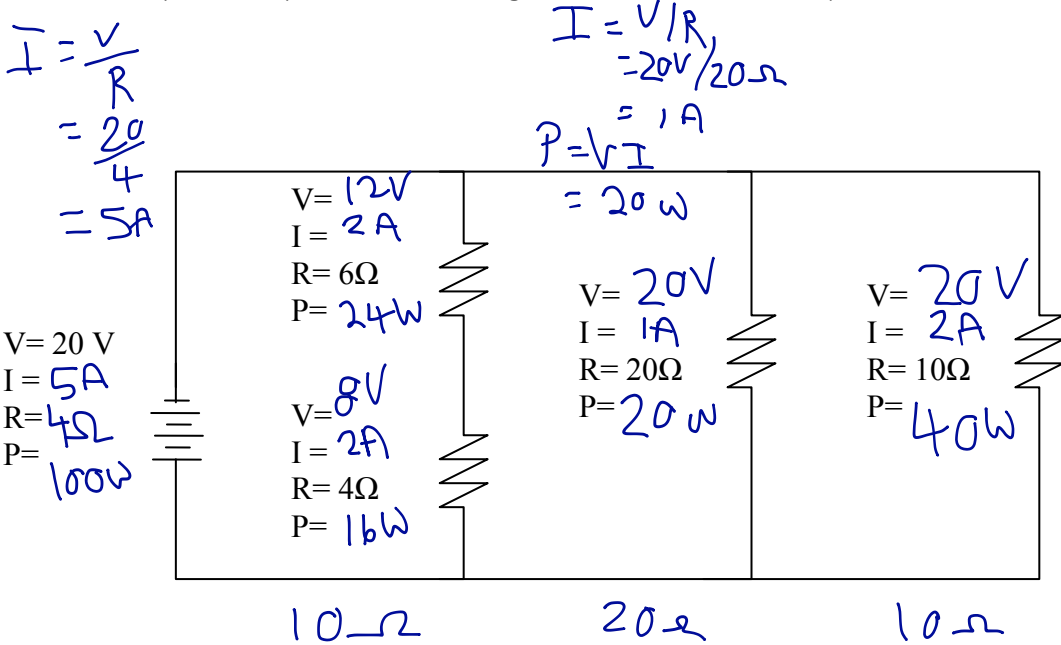8. Complete the parallel circuit diagram shown below. Show your work. (10 marks)



$$\frac{1}{R_{eq}} = \frac{1}{10} + \frac{1}{20} + \frac{1}{10}$$


$$= \frac{2}{20} + \frac{1}{20} + \frac{2}{20}$$

$$\frac{1}{R_{eq}} = \frac{5}{20} \therefore R_{eq} = 20/5$$

$$R_{eq} = 4\Omega$$

/ 13	C2.3	I can state Kirchoff's laws and Ohm's law, and use them to explain direct current, potential difference, and resistance in mixed circuit diagrams.
------	------	--

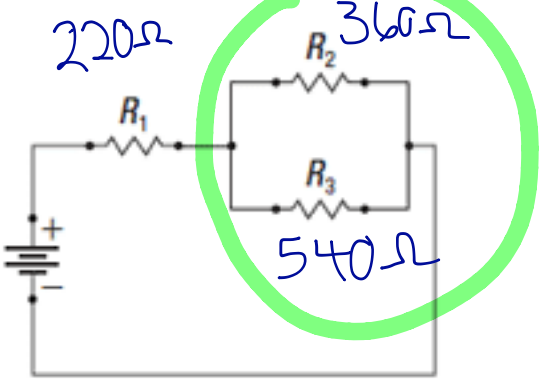9. Calculate the total resistance for the circuit pictured below.  $R_1=220\Omega$ ,  $R_2=360\Omega$ , and  $R_3=540\Omega$ . (3 marks)



$$\frac{1}{R_{eq}} = \frac{1}{360} + \frac{1}{540}$$

$$= \frac{3}{1080} + \frac{2}{1080}$$

$$\frac{1}{R_{eq}} = \frac{5}{1080}$$

$$R_{eq} = 1080/5 = 216\Omega$$

$$R_T = 220\Omega + 216\Omega$$

$$= 436\Omega$$

$$= 440\Omega \text{ (2 sig figs)}$$

10. Analyze the following circuit. Determine  $R_T$ ,  $I_T$ ,  $V_1$ ,  $V_2$ ,  $V_3$ ,  $I_1$ ,  $I_2$ , and  $I_3$ . (10 marks)

$$V_1 = V_2 = 120V - 90V$$


$$= 30V$$

$$V_T = 120V$$

$$R_T = 20\Omega$$

$$I_T = \frac{120V}{20\Omega}$$

$$I_T = 6A$$

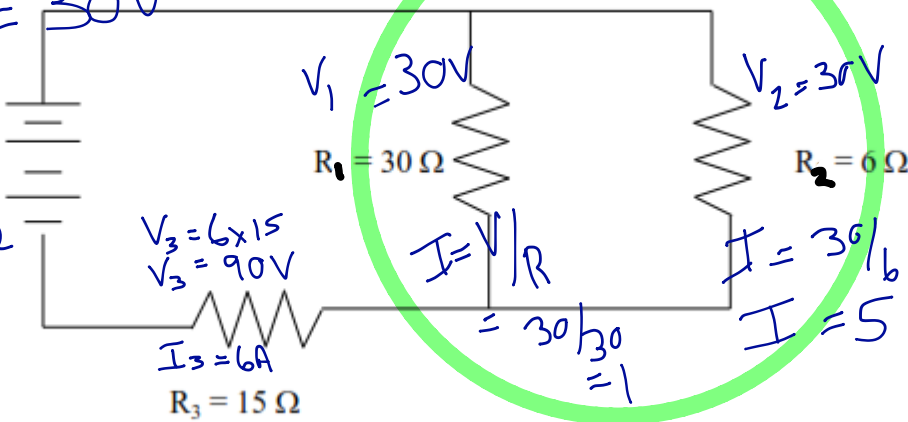

	V	I	R
Total	120	6	20
1	30	1	30Ω
2	30	5	6Ω
3	90	6	15Ω

$$R_T = 15\Omega + 5\Omega$$

$$R_T = 20\Omega$$

$$\frac{1}{R_{eq}} = \frac{1}{30} + \frac{1}{6}$$

$$= \frac{1}{30} + \frac{5}{30}$$

$$\frac{1}{R_{eq}} = \frac{6}{30}$$

$$R_{eq} = 30/6$$

$$R_{eq} = 5\Omega$$